

## Power Supply Circuits

- Power distributed in the form of AC
- Many electrical devices are DC & operate at lower voltages.
- Wall outlets are 110 V ; this is an RMS voltage

### RMS Voltage

We want to be able to easily calculate power loss due to resistive loads,

$$P_{\text{loss}}(t) = i^2(t) R$$

$$P_{\text{loss Ave}} = \frac{1}{T} \int_0^T i^2(t) R dt$$

$$i^2 R = \frac{v^2}{R}$$

$\therefore$

$$\begin{aligned} P_{\text{loss ave}} &= \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt \\ &= \frac{1}{R} \left[ \frac{1}{T} \int_0^T v^2(t) dt \right] \end{aligned}$$

Define

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Now

Now

$$P_{\text{loss ave}} = \frac{V_{\text{RMS}}^2}{R}$$

For AC,


$$v(t) = v_0 \cos(\omega t + \phi)$$

$$\begin{aligned} \therefore V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T v_0^2 \cos^2(\omega t + \phi) dt} \\ &= v_0 \sqrt{\frac{1}{T} \int_0^T \cos^2(\omega t + \phi) dt} \\ &= v_0 \sqrt{\frac{1}{2}} \end{aligned}$$

$$V_{\text{RMS}} = v_0 \frac{1}{\sqrt{2}}$$

$v_0$  = peak voltage

$$v_0 = \sqrt{2} V_{\text{RMS}}$$

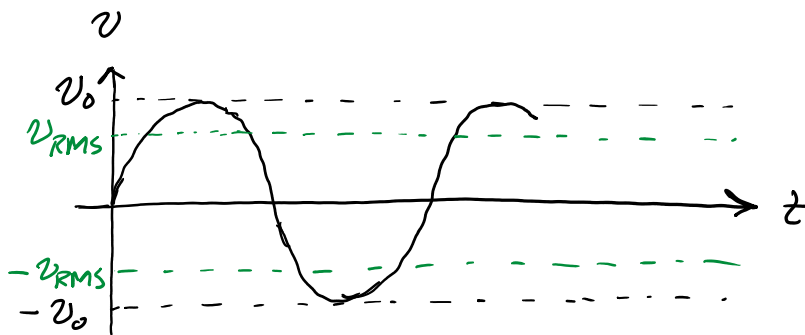

How to convert AC power (110 Vac) to DC power (5V)?


Design of a power supply circuit can be broken down into 3 problems:

1. Voltage reduction


1. Voltage reduction
2. AC to DC conversion
3. Voltage regulation

Problem 1: Voltage reduction

Use stepdown transformer

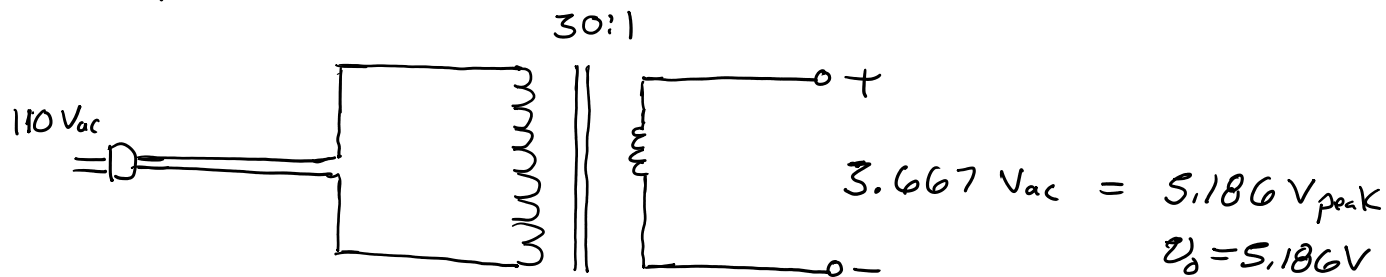



Problem 2: AC to DC conversion

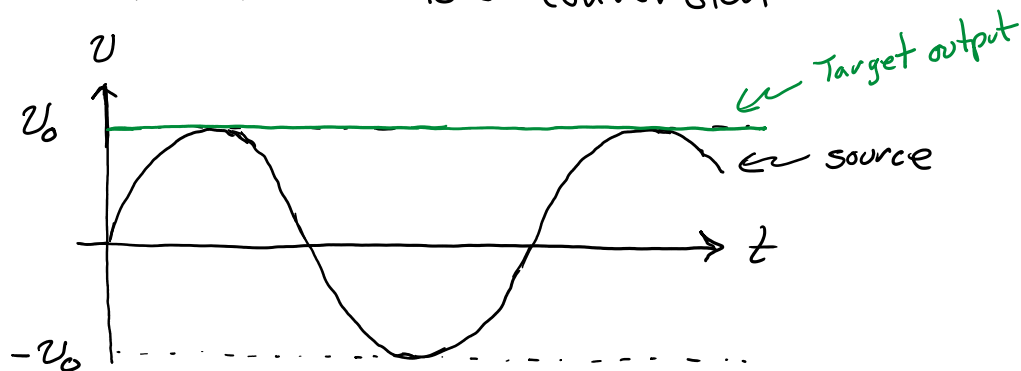



A number of strategies have been devised  
 We'll explore basic methods:


1. Half-wave rectification
2. " " " with filtering
3. Full-wave rectification
4. " " " with filtering

## Half-Wave Rectifier :

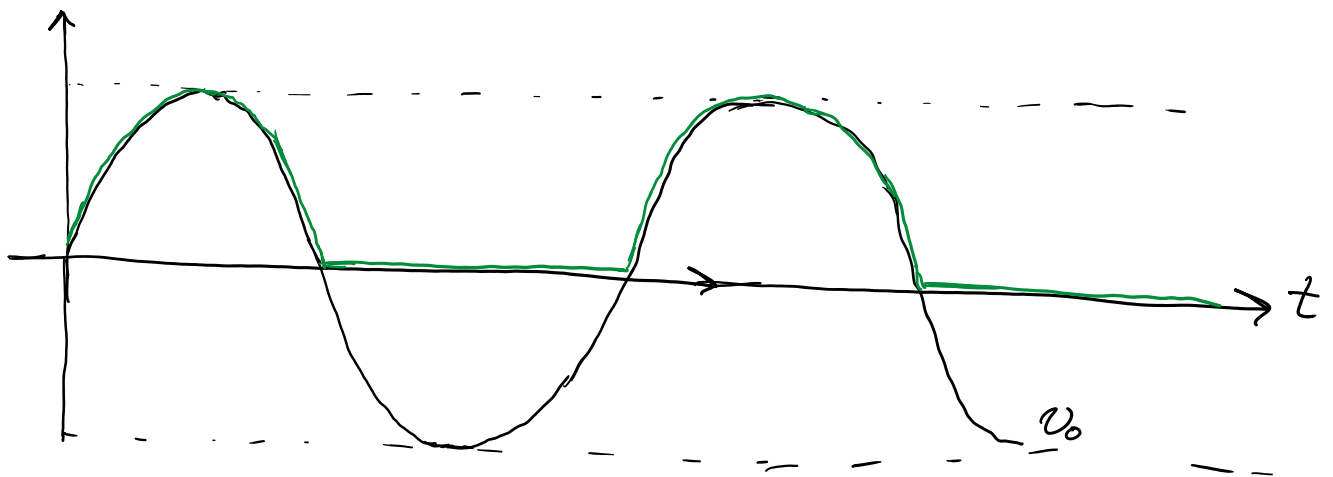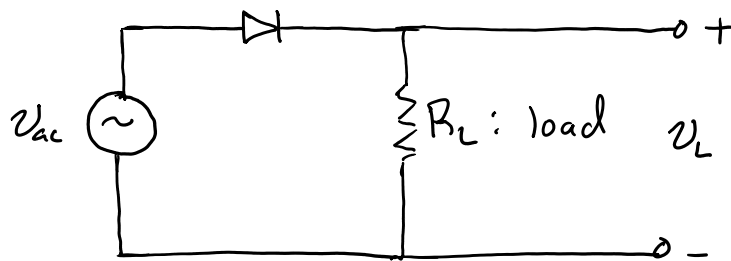

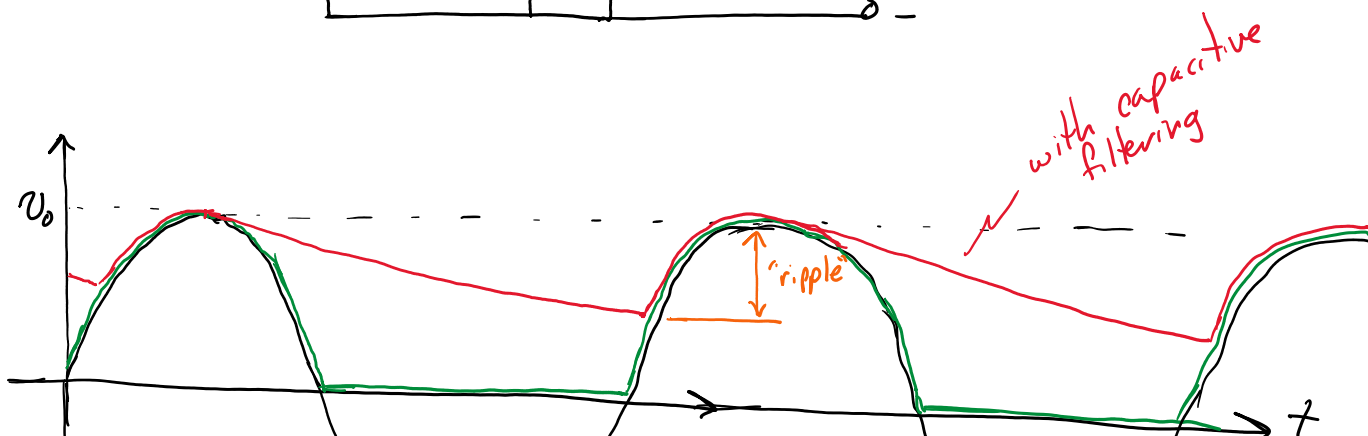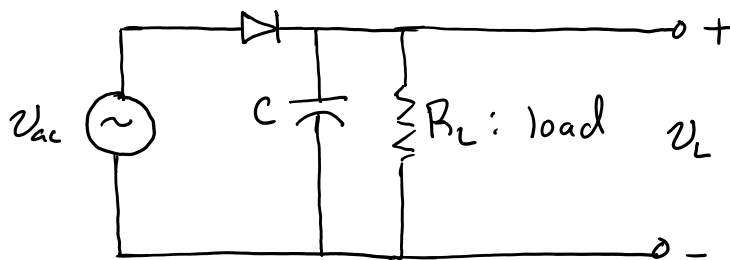We can improve this with capacitive filtering.





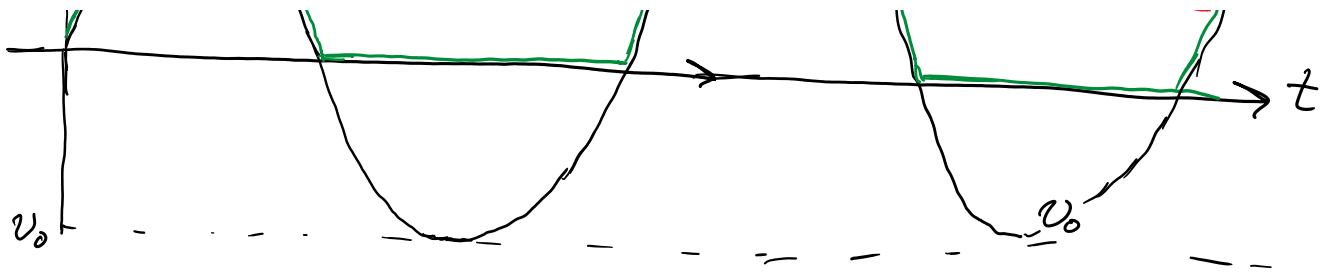

Increasing  $C$  reduces ripple because the capacitor can store more energy.

Increasing  $R_L$  reduces ripple because the load draws less current.



Full-wave Rectifier:

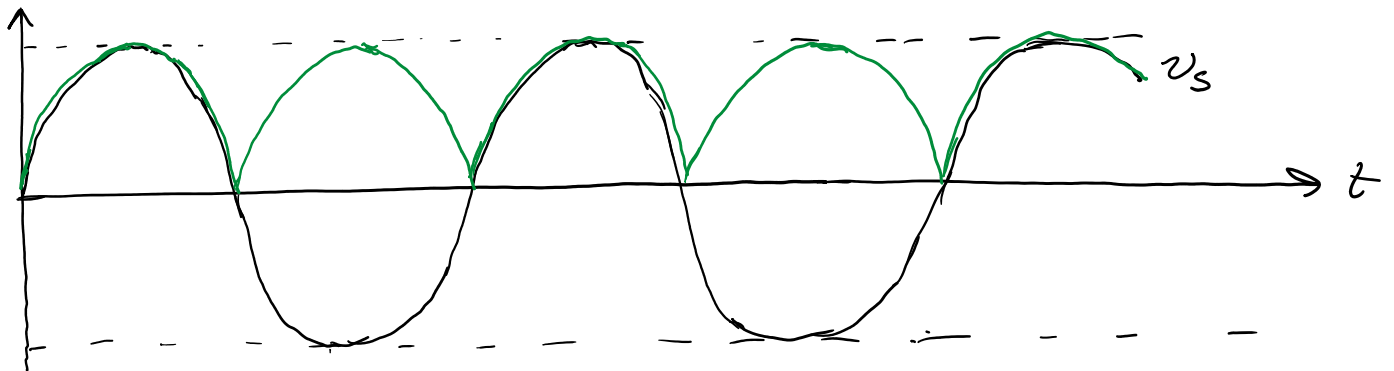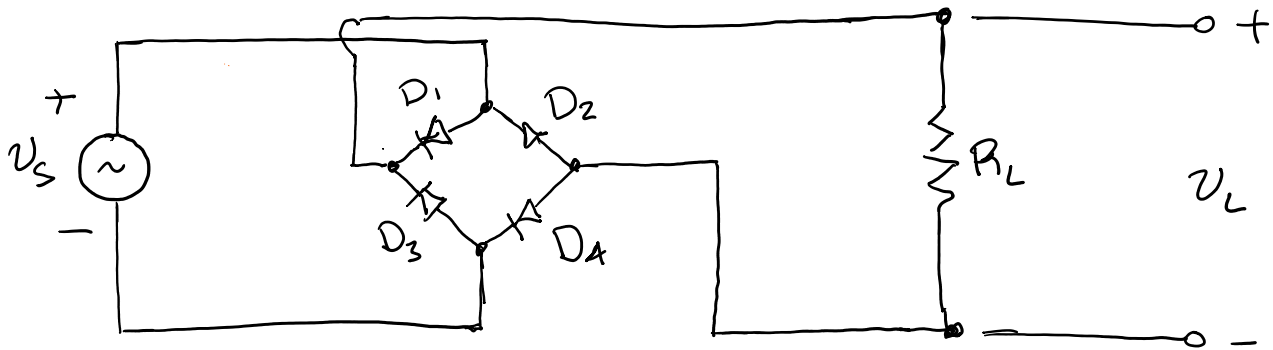

Can improve with capacitive filtering




Can improve with capacitive filtering

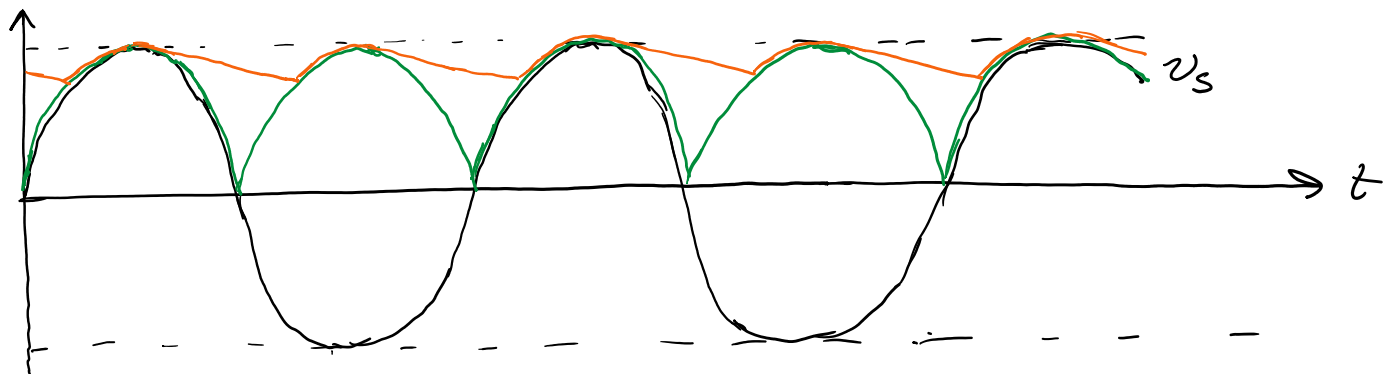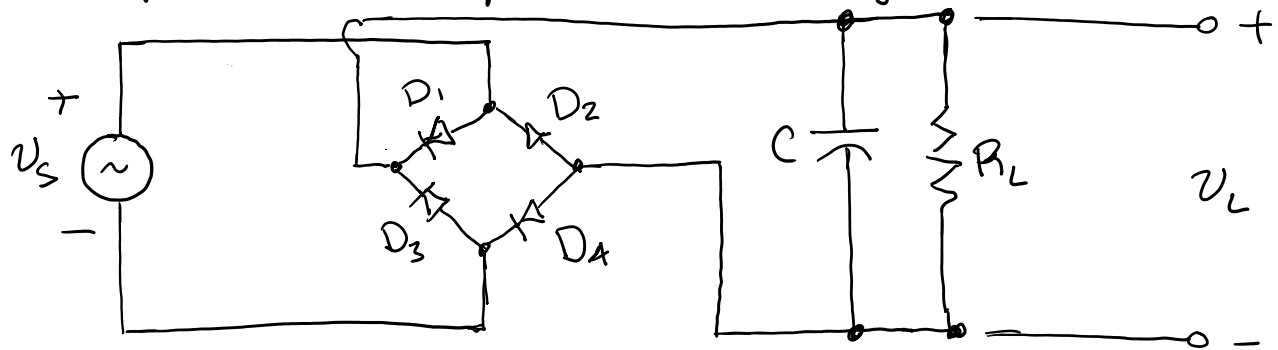



Shunt Voltage Regulator:

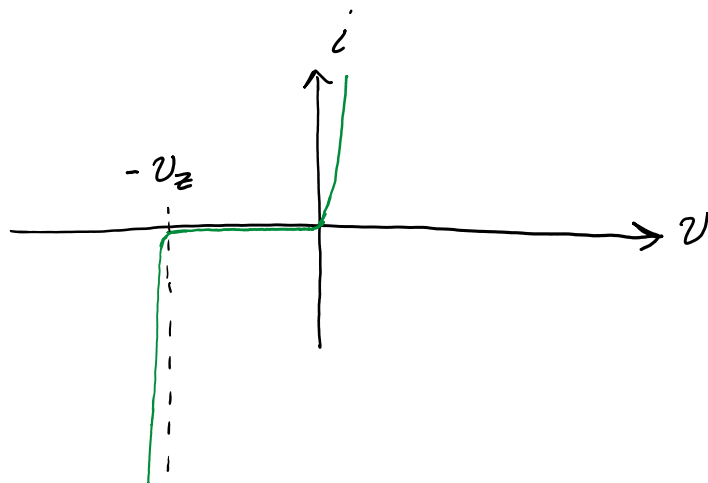Recall current-voltage relation for a diode




A "zener" diode is a diode designed to be operated in reverse. They're built to provide a

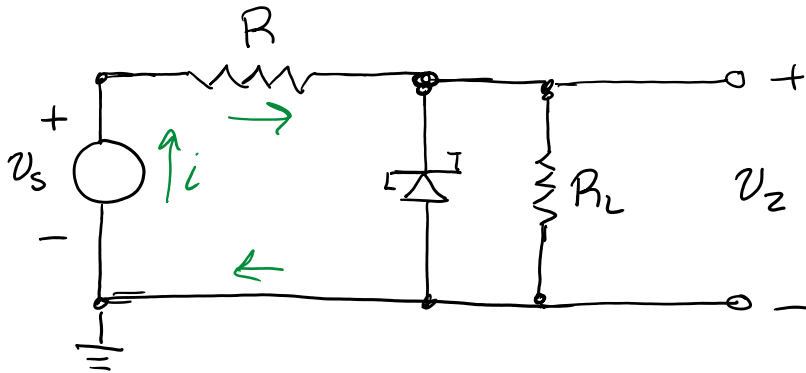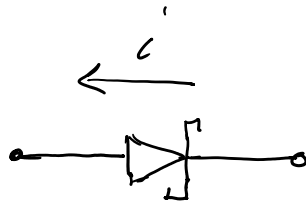operated in reverse. They're built to provide a specific  $V_Z$  value.



Emitter-follower voltage reg.

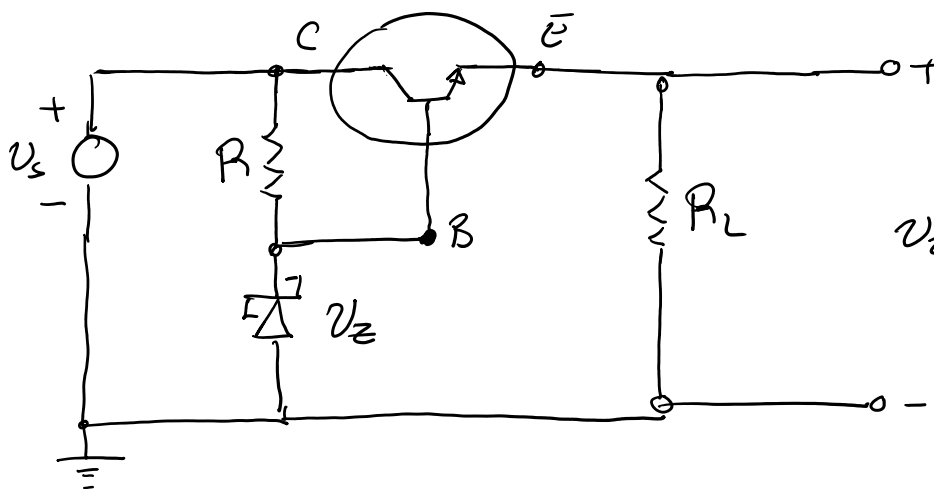

$v_z + v_{BE}$  ;  $v_{BE} \cong$  activation voltage