

Transient Circuit Analysis

Want to consider how circuits respond to a sudden change; e.g. toggling a switch.



Circuit response is non-trivial when circuit elements capable of storing energy are present.

Two common examples of circuit elements capable of storing energy are:

- Capacitor
- Inductor

Capacitors

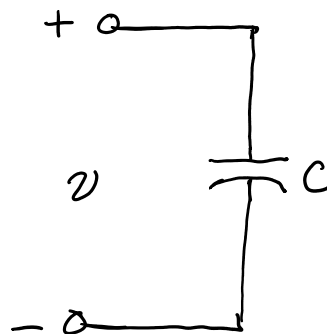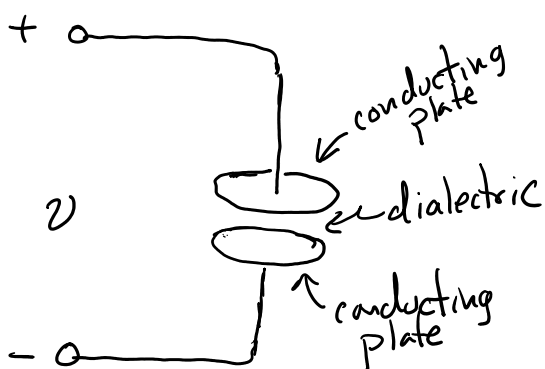A capacitor is a circuit element that consists of two conducting surfaces separated by a dielectric material (insulator).



The charge on the capacitor is proportional to the voltage potential between the two plates

the charge on the capacitor is proportional to the voltage potential between the two plates

$$q = CV$$

where C is the "capacitance" and has the units

$$\text{Farad} = \frac{\text{Coulomb}}{\text{Volt}}$$

Typical capacitors have a capacitance $\sim \mu\text{F}$.

Recall: $i = \frac{dq}{dt}$

\therefore


$$i_c = \frac{d}{dt}(CV_c) \Rightarrow$$

$$i_c = C \frac{dv_c}{dt}$$

Remarks: ^{circuit}


- In a DC ^{circuit}, there is no current flow to/from the capacitor. The capacitor acts like an open switch.
- current does not flow through the capacitor. current flows from one plate to the other via the connecting circuit.

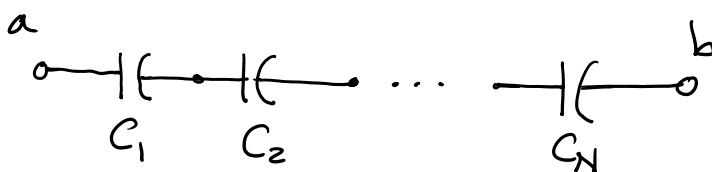capacitors in series: Can show using KVL,




a b



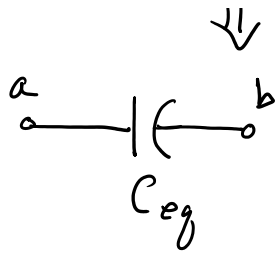

$$C_{eq} = \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right]^{-1}$$

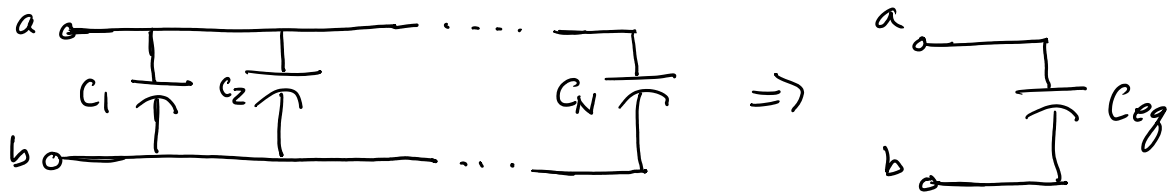Capacitors in parallel: Can show using KCL



$$C_{eq} = C_1 + C_2 + \dots + C_N$$

* Opposite of how resistors combine!

Energy storage:

Recall $p(t) = v(t) i(t)$

Energy in capacitor = work done on capacitor = integral of power


$$\begin{aligned} e(t) = w(t) &= \int_0^t p(x) dx = \int_0^t v(x) \left[C \frac{dv}{dx} \right] dx \\ &= \frac{1}{2} C v^2(t) \end{aligned}$$

units: Joules

Inductors

An inductor is a circuit element consisting of a conducting wire wound around a core. The core may be nonmagnetic or ferromagnetic (iron).

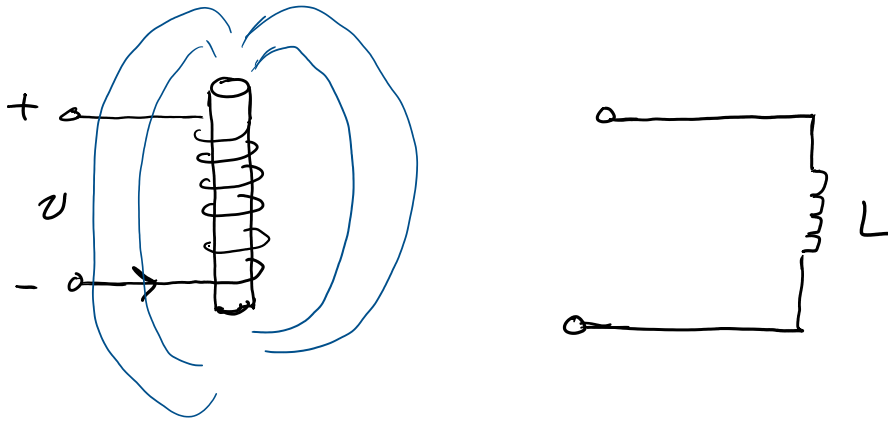core may be nonmagnetic or ferromagnetic (iron).



As current flows through the wire, a magnetic field forms. If core is nonmagnetic, the magnetic field will extend beyond the inductor. If a ferromagnetic core is used, the magnetic field will be contained in the core.

Joseph Henry discovered,

$$v(t) = L \frac{di}{dt}$$


where L is the "inductance" and has the unit "Henry"

$$\text{Henry} = \frac{\text{Volt} \cdot \text{second}}{\text{Amp}}$$

Typical inductors range from $\sim \mu\text{H}$ to $\sim 10\text{H}$.



Inductors in series: use KVL,



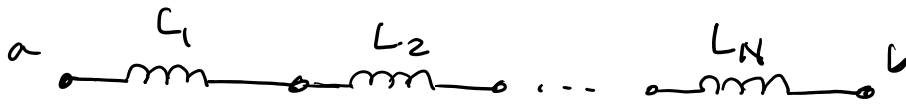

$$L_{eq} = L_1 + L_2 + \dots + L_N$$

Inductors in parallel: Use KCL,

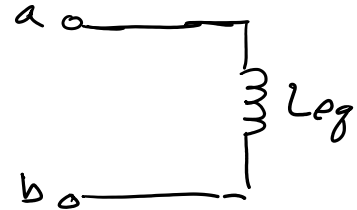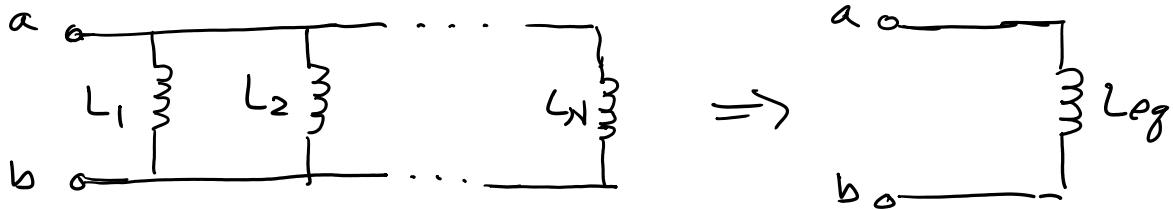

$$L_{eq} = \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right]^{-1}$$

Combine like resistors.

Energy storage:

Apply $p(t) = v(t) i'(t)$

$$\begin{aligned} e(t) = w(t) &= \int_0^t \left[L \frac{di}{dx} \right] i(x) dx \\ &= L \int_0^t i(x) \frac{di}{dx} dx \\ &= \frac{1}{2} L i^2(t) \end{aligned}$$