

Introduction to Electric Circuits

ENAE 362

Dr. Benjamin S. Silbaugh

University of Maryland

Fall 2024



Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

What do you remember about charge?

Charge, q

- ▶ Fundamental property of matter
- ▶ Conserved quantity: charged is neither created or destroyed
- ▶ Two types: positive and negative
- ▶ Like charges repel, opposite charges attract
- ▶ Units: Coulombs, C
- ▶ Charge is quantized; smallest unit of charge is the electron
- ▶ A single electron has a negative charge of $-1.602 \times 10^{-19}C$

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

What do you remember about current?

Current, i

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws


“Current” is charge in motion.

$$i = \frac{dq}{dt}$$

- ▶ Units: Amperes, A
- ▶ Often abbreviate Amperes as Amp
- ▶ $1 \text{ A} = 1 \text{ C/s}$
- ▶ Sign convention: i is positive in the direction positive charge movement

Current flow through battery

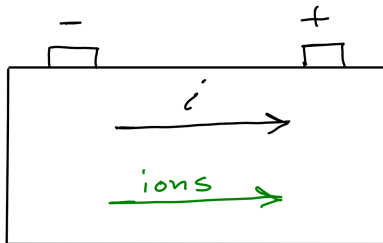In electrochemical batteries, current flow is due to the movement of positive ions.



Charge

Current

Voltage


Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Current flow through a wire

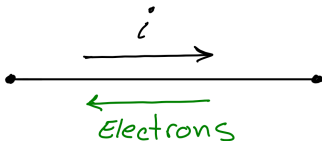Current flow through a wire is due to the movement of electrons. Electrons carry negative charge. Thus, the direction of positive current flow is in the opposite direction of electron flow.



NOTE:

- ▶ In circuit analysis, the effect of electron motion is equivalent to the movement of positive charge in the opposite direction.
- ▶ In your lab manuals, the author sometimes chooses to draw current flow in the direction of electron movement.

Range of Current

Typical orders of magnitude in Amps

10^{-12}	Synaptic current in brain cells
10^{-8}	Current in computer memory
10^{-3}	Threshold of sensation in humans
10^{-1}	Fatal to humans
10^1	Common household appliances (vacuum cleaners)
10^3	Large industrial motors
10^4	Lightning bolt

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

What do you remember about voltage?

Voltage, v

“Voltage” is an electric potential directly related to the motive force required to move charge through a conductor.

- ▶ Voltage is to current as pressure is to mass flow rate.
- ▶ Always measured relative to some reference point; never work with absolute values of voltage.
- ▶ Units: Volt, V

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Range of Voltage

Typical orders of magnitude in Volts:

10^{-8}	Antenna of radio receiver
10^{-6}	Voltage between two points on human scalp
10^{-3}	Voltage produced by heart across human chest
10^0	Common DC electronics (1.5 V - 12 V)
10^2	House wiring (120V)
10^3	Large industrial motors
10^5	Cross-country transmission lines
10^8	Lightning

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Lumped Circuit Modelling

In this class, we will assumed a “lumped circuit model.”

- ▶ Idealize circuit as a network of “elements” connected by ideal conductors.
- ▶ Each circuit element has a well defined input-output behavior
- ▶ Ignore the possibility of interference between circuit elements
- ▶ Real-world circuit components are represented by one or more idealized circuit elements.
 - ▶ Real-world resistance of electrical connections will be modeled by a resistor circuit element.
 - ▶ A light bulb can be modeled as a resistor

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Basic types of circuit elements

Charge

Current

Voltage

**Lumped Circuit
Modeling**

Circuit Topology

Circuit Laws


- ▶ Active elements
 - ▶ Independent sources
 - ▶ Dependent sources
- ▶ Passive elements

Active Element: Independent sources

Voltage source (e.g. battery, generator):





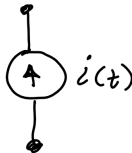Current source (e.g. photovoltaic cells, LED driving circuit):





Active Element: Dependent Sources

Voltage sources:

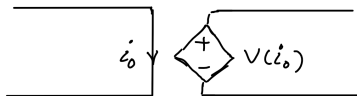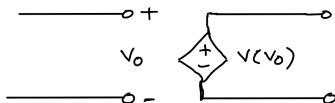



Current sources:

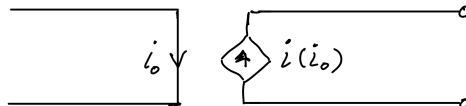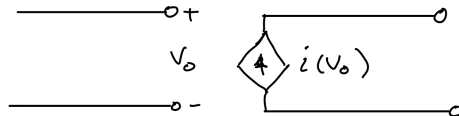



We'll encounter this type of circuit element when discussing operational amplifiers.
Don't worry too much about this now.

Active Element: Dependent Sources

Voltage sources:

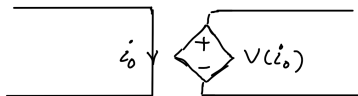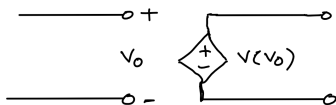

Current sources:

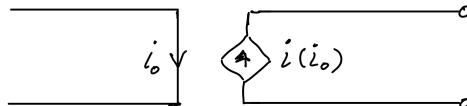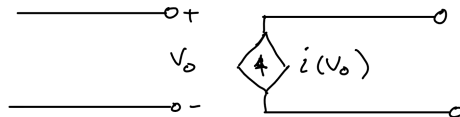

We'll encounter this type of circuit element when discussing operational amplifiers.
Don't worry too much about this now.

Passive Elements

Common examples of passive elements:


- ▶ Resistor, $v = iR$



- ▶ Inductor, $v = L \frac{di}{dt}$



- ▶ Capacitor, $i = C \frac{dv}{dt}$


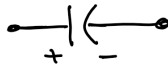


We'll discuss these more later.

Circuit Topology

- ▶ “Topology” is a branch of geometry that concerns itself with how things are connected (or not connected). It is what remains after to remove dimensional quantities like size and shape.
- ▶ In (lumped) circuit analysis, we only care about the topology of a circuit; i.e. how elements are connected.
- ▶ Basic topological elements of a circuit: node, branch, loop, and mesh

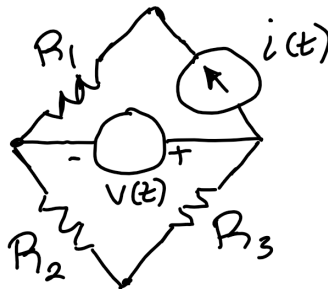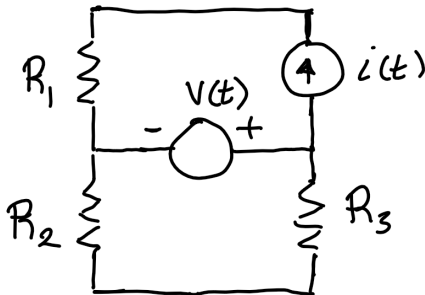
Example: Are these two circuits the same?



Node

A circuit “node” is a point of connection between two or more circuit elements.


Example: How many nodes?

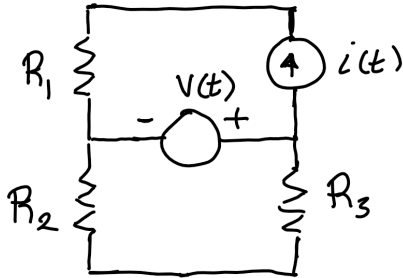

Loop

A circuit “loop” is any closed path through a circuit in which no node is crossed more than once.


Example: How many loops?

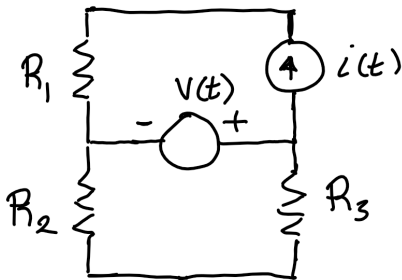

Mesh

A circuit “mesh” is any loop that does not contain another loop.


Example: How many meshes?

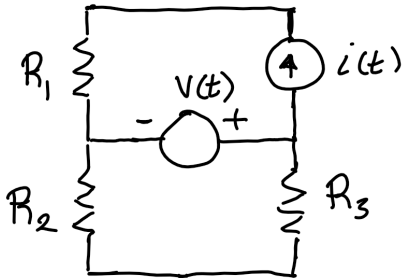

Branch

A circuit “branch” is a portion of the circuit containing only a single element and the nodes at each end of the element.

Example: How many branches?

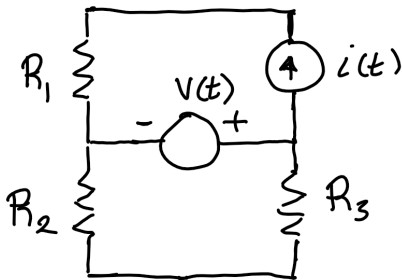

Circuit Laws

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Laws governing the behavior of a circuit:


1. Ohm's Law
2. Kirchhoff's First Law
3. Kirchhoff's Second Law

Ohm's Law

The voltage across a resistance is directly proportional to the current flowing through it.

- ▶ Resistance is measured in Ohms, Ω
- ▶ $1\Omega = 1\text{ V/A}$

$$v = iR$$

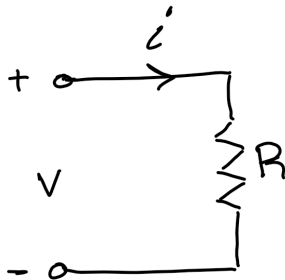

Power loss due to resistance

Power

$$P = vi$$

Substitute Ohm's Law, $v = iR$,

$$\begin{aligned} P &= vi \\ &= (iR)i \\ &= i^2 R \end{aligned}$$

or

$$\begin{aligned} P &= vi \\ &= v(v/R) \\ &= \frac{v^2}{R} \end{aligned}$$

Charge

Current

Voltage

Lumped Circuit
Modeling

Circuit Topology

Circuit Laws

Kirchhoff's First Law

The algebraic sum of the currents entering any node is zero.


$$\sum_j i_j = 0$$

Also known as Kirchhoff's Current Law (KCL).

NOTE: When applying KCL, it is often easier think in terms of

$$\sum_{in} i - \sum_{out} i = 0$$

Example:

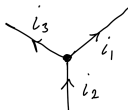


$$i_2 - i_1 - i_3 = 0$$

Kirchhoff's Second Law

The algebraic sum of voltages around any loop is zero.

Also known as Kirchhoff's Voltage Law (KVL)

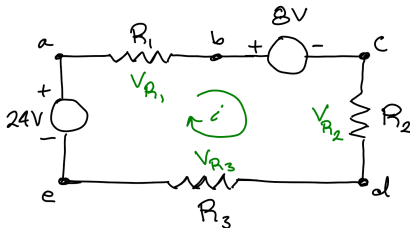Example: Assuming clockwise current flow...



$$-v_{R_1} - 8V - v_{R_2} - v_{R_3} + 24V = 0$$