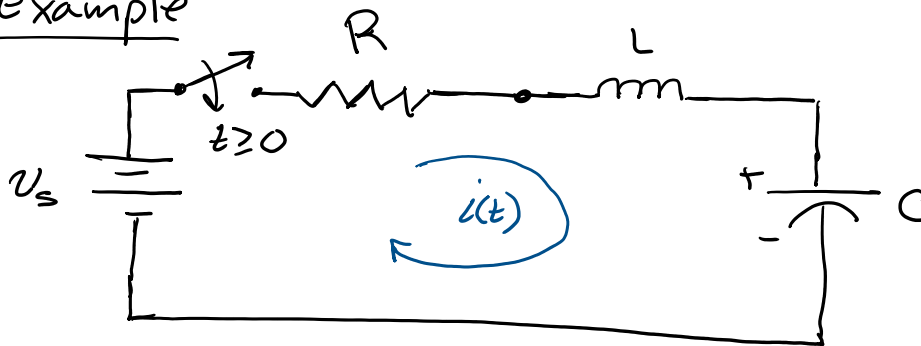


2nd Order Circuits

When two different types of energy storage elements are present in a circuit, the circuit will exhibit a 2nd order transient response when there is a change to one of its inputs.

Example



Find current flow as a function of time.

Apply KVL,

$$(1) \quad V_s - iR - v_L - v_C = 0$$

Recall

$$(2) \quad v_L = L \frac{di}{dt}$$

$$(3) \quad i_C = C \frac{dv_C}{dt} \Rightarrow \frac{dv_C}{dt} = \frac{1}{C} i_C$$

Differentiate (1),

$$\cancel{\frac{dV_s}{dt}} - \frac{di}{dt} R - \frac{dv_L}{dt} - \frac{dv_C}{dt} = 0$$

$$\overset{0^k}{\Rightarrow} \frac{di}{dt} R + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

This is a linear, 2nd order, homogeneous ODE.

$$\frac{d^2 y}{dt^2} + y = 0$$

$$\Rightarrow \frac{d^2 y}{dt^2} = -y$$

Fundamental solution

$$i(t) = K e^{st}$$

Substitute into ODE,

$$s^2 K e^{st} + \frac{R}{L} s K e^{st} + \frac{1}{LC} K e^{st} = 0$$

$$\Rightarrow \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) K e^{st} = 0$$

$$\Rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad \text{for nontrivial solution!}$$

$$\therefore s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Two fundamental solutions.

The general solution is the linear combination of the fundamental solutions!

$$i(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

If $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$: $s_{1,2}$ are real and distinct

$$i(t) = K_1 e^{\left(-\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}\right)t} + K_2 e^{\left(-\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}\right)t}$$

Apply initial conditions to find K_1, K_2

Response is an exponential decay from some initial state

We call this an "overdamped" system


If $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$: $s_{1,2}$ are complex and distinct

$$s_{1,2} = -\frac{R}{2L} \pm j \underbrace{\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}}_{\omega} ; \quad j = \sqrt{-1}$$

$$\therefore i(t) = e^{-\frac{R}{2L}t} \left[K_1 e^{j\omega t} + K_2 e^{-j\omega t} \right]$$

Recall Euler's identity
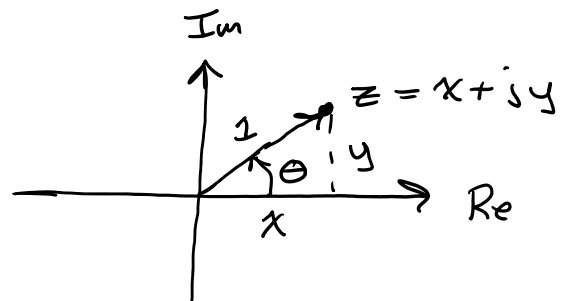
$$e^{j\theta} = \cos\theta + j\sin\theta$$




\therefore

$$i(t) = e^{-\frac{R}{2L}t} \left[A_1 \cos(\omega t) + A_2 \sin(\omega t) \right]$$

or rewrite in amplitude and phase form
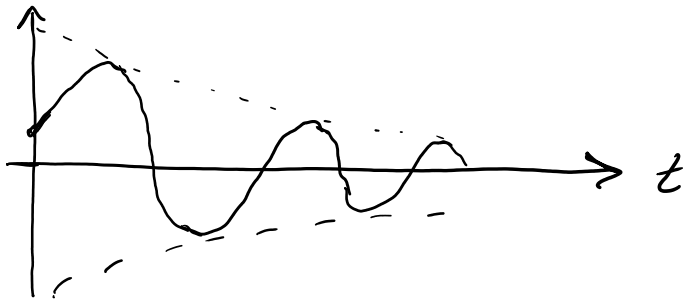
$$i(t) = e^{-\frac{R}{2L}t} A \cos(\omega t + \phi)$$



Decaying oscillation

We call this an "underdamped" system

If $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$: $S_{1,2}$ are real & repeated

$$S_1 = S_2 = -\frac{R}{2L}$$

$$i(t) = K_1 e^{-\frac{R}{2L}t} + K_2 t e^{-\frac{R}{2L}t}$$

We call this a "critically damped" system