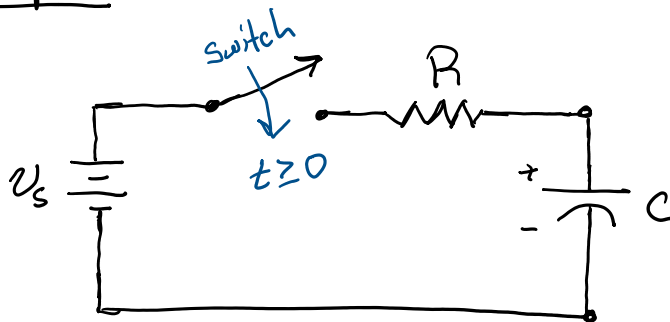


First Order Circuits

A circuit consisting of a single energy storage element (e.g. capacitor or inductor) will exhibit a 1st order transient response when there is a change to one of the circuit inputs (e.g. toggling a switch).

Example: Consider



Circuit begins from an equilibrium state.

Find

- Formulate governing equation
- Determine system response

Solution

- Guess a clockwise current flow and apply KVL

$$(1) \quad v_s - iR - v_c = 0$$

Recall,

$$(2) \quad i_c = C \frac{dv_c}{dt}$$

Take $\frac{d}{dt}$ of eq (1) and substitute (2),

$$\frac{dv_s}{dt} - \frac{di}{dt} R - \frac{dv_c}{dt} = 0$$

$$\cancel{\frac{dV_c}{dt}} - \frac{di}{dt} R - \frac{dV_c}{dt} = 0$$

$$\Rightarrow \frac{di}{dt} R + \frac{dV_c}{dt} = 0$$

$$\Rightarrow \frac{di}{dt} R + \frac{1}{C} i = 0$$

$$\Rightarrow \boxed{\frac{di}{dt} + \frac{1}{RC} i = 0} \quad (3)$$

b) Rewrite (3) as

$$\frac{di}{i} = -\frac{1}{RC} dt$$

Integrate

$$\int \frac{1}{i} di = -\frac{1}{RC} \int dt$$

$$\Rightarrow \ln i = -\frac{1}{RC} t + K_1$$

$$\Rightarrow i(t) = K_2 e^{-t/RC}$$

Apply Initial Conditions (IC's),

$$i(0) = i_0 = K_2$$

$$\therefore i(t) = i_0 e^{-t/RC}$$

Also find $V_c(t)$

$$i = C \frac{dV_c}{dt}$$

$$\Rightarrow \int dV_c = \frac{1}{C} \int i dt$$

$$\Rightarrow V_c(t) = \frac{1}{C} \int i_0 e^{-t/RC} dt$$

$$\Rightarrow v_c(t) = \frac{1}{C} \int i_0 e^{-t/RC} dt$$

$$\Rightarrow v_c(t) = -\frac{i_0}{C} RC e^{-t/RC} + K$$

$$\Rightarrow v_c(t) = -i_0 R e^{-t/RC} + K$$

Apply IC's,

$$v_c(0) = v_{c0} = -i_0 R + K$$

$$\Rightarrow K = v_{c0} + i_0 R$$

Apply KVL at $t=0$

$$v_s - i_0 R - v_{c0} = 0$$

$$\Rightarrow v_s = v_{c0} + i_0 R$$

\therefore

$$K = v_s$$

\therefore

$$v_c(t) = v_s - i_0 R e^{-t/RC}$$

What is i_0 ? By KVL,


$$i_0 R = v_s - v_{c0}$$

\therefore

$$v_c(t) = v_s - (v_s - v_{c0}) e^{-t/RC}$$

If $v_{c0} = 0$ then
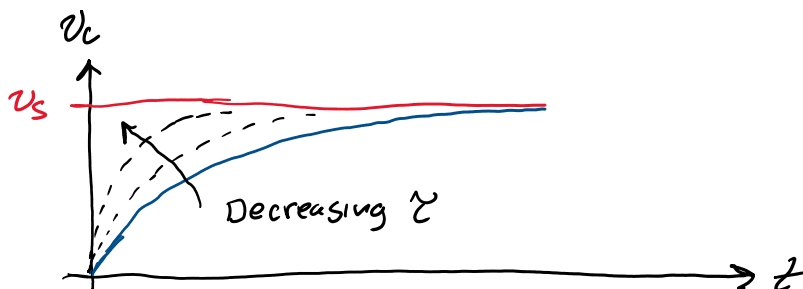
$$v_c(t) = v_s [1 - e^{-t/RC}] = v_s [1 - e^{-\frac{t}{\tau}}] ; \tau = RC$$




We call the parameter τ the "time constant"

We call the parameter τ the "time constant"

Large $\tau \Rightarrow$ slow response, takes longer to reach equilibrium


Large $C \Rightarrow$ more charge is needed to fill capacitor

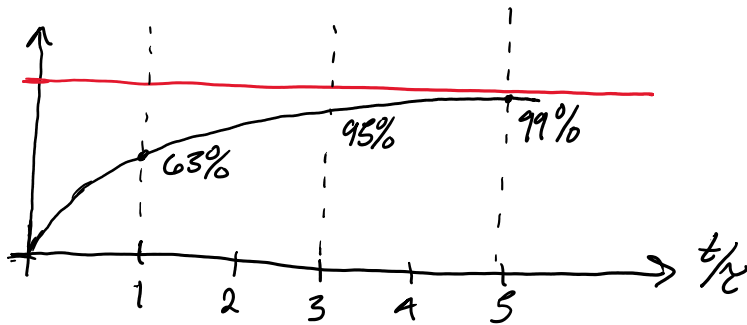Large $R \Rightarrow$ reduces current flow, takes longer for charge to fill capacitor



In practice, the circuit reaches equilibrium in $\sim 5\tau$.

Example

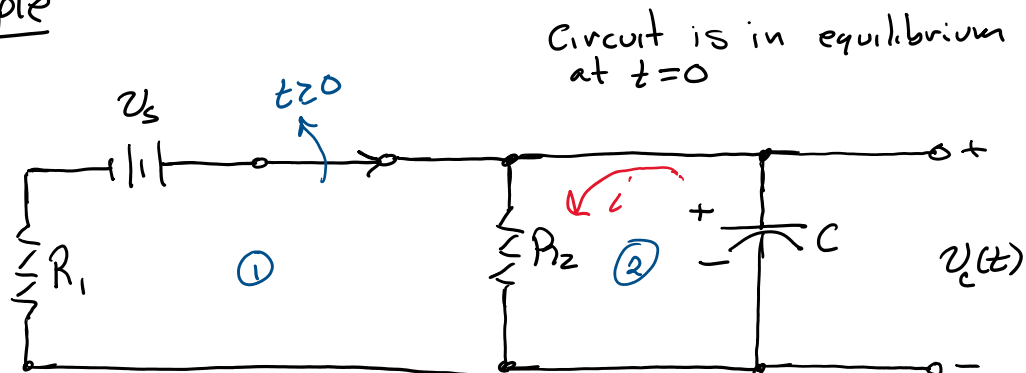

Find $V_C(t)$

Solution

Since circuit starts from equilibrium with a closed switch, the initial voltage across the capacitor $V_C(0)$ must equal voltage across R_2 .

To get governing equation, apply KVL to mesh 2

To get governing equation, apply KVL to mesh 2
(no current flow in mesh 1 when switch is open).

$$v_c - i R_2 = 0$$

$$\Rightarrow \frac{dv_c}{dt} - \frac{di}{dt} R_2 = 0$$

$$\Rightarrow -\frac{1}{C} i - \frac{di}{dt} R_2 = 0$$

$$\Rightarrow \frac{di}{dt} + \frac{1}{CR_2} i = 0$$

Note:

$$i_c = C \frac{dv_c}{dt} \Rightarrow$$


Since we chose ccw current flow in our analysis, we must flip sign

$$i = -i_c$$

Same equation as before