

## Transistors


A type of semiconductor used for a very wide range of applications.

We'll focus on two types:

1. NPN
2. MOSFET
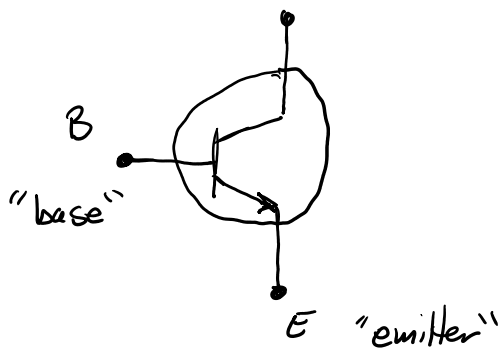
### NPN transistor


May be used as a switch or as a current amplifier.



3 modes of operation:

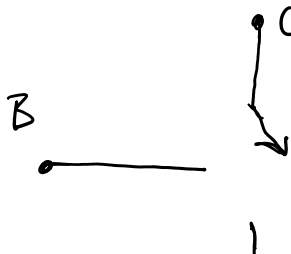
1. Cut off
2. Active
3. Saturation

Cutoff mode: When the voltage potential between base and emitter,  $V_{BE}$ , is below  $V_F$ , the activation threshold, the NPN acts like an open switch between collector & emitter.




Typically

$$V_F \approx 0.7 \text{ V}$$

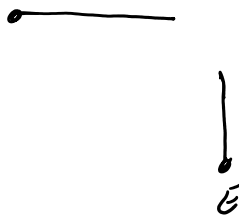

$$V_F \approx 0.7 \text{ V}$$

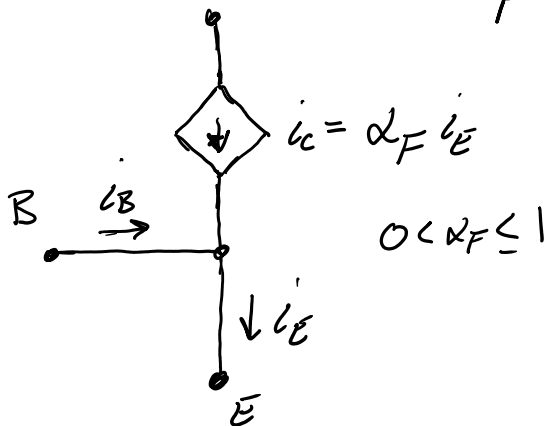Active mode: When  $V_{BE} > V_F$  and the current flow is below the threshold for saturation, then NPN goes into the "active state" and acts like a current amplifier.



KCL:


$$i_B + i_C - i_E = 0$$

$$\Rightarrow i_B + \alpha_F i_E - i_E = 0$$

$$\Rightarrow i_B + (\alpha_F - 1) i_E = 0$$

$$\Rightarrow \frac{i_E}{i_B} = \frac{1}{1 - \alpha_F} > 1$$

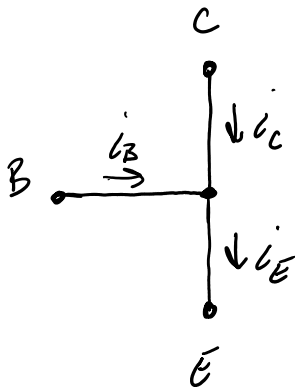Saturation mode: When  $i_B$  reaches the saturation threshold of the NPN, the NPN acts like a closed switch.



What is the saturation threshold,  $i_{B \text{ sat}}$ ?

Saturation occurs when  $i_C$  reaches the "closed switch"

Saturation occurs when  $i_c$  reaches the "closed switch" current flow.

Apply KCL:

$$i_B + i_c - i_E = 0$$

If we're at the threshold for saturation,

$$i_c = \alpha_F i_E \Rightarrow i_E = \frac{1}{\alpha_F} i_c$$

$\therefore$

$$i_B + i_c - \frac{1}{\alpha_F} i_c = 0$$

$$\Rightarrow i_B + \left(1 - \frac{1}{\alpha_F}\right) i_c = 0$$

$$\Rightarrow i_B = \frac{1 - \alpha_F}{\alpha_F} i_c$$

$$i_B = -\left(1 - \frac{1}{\alpha_F}\right) i_c$$

$$= -\left(\frac{\alpha_F - 1}{\alpha_F}\right) i_c$$

$$\Rightarrow i_B = \left(\frac{1 - \alpha_F}{\alpha_F}\right) i_c$$

If saturated, the  $i_c$  equals  $i_{c,sat}$ , which is equal to the closed switch current flow into collector.

$$i_{B,sat} = \frac{1 - \alpha_F}{\alpha_F} i_{c,sat}$$


Depends on the external circuit

Define


$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{i_c}{i_B} : \text{Forward common emitter transfer ratio.}$$

Example: Switching a light bulb


$$\beta_F = 50$$

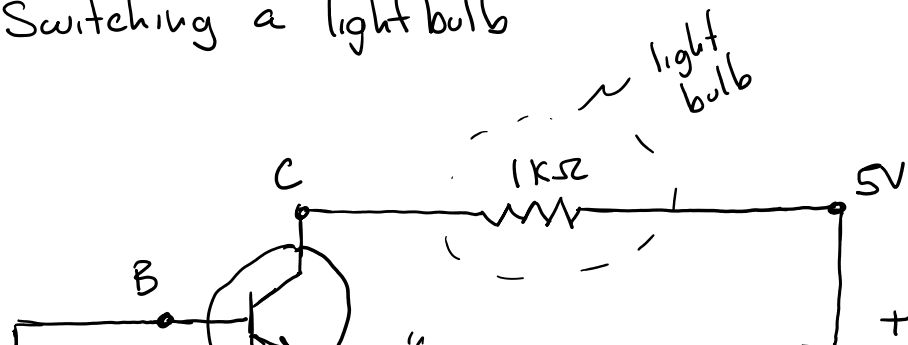

1.1

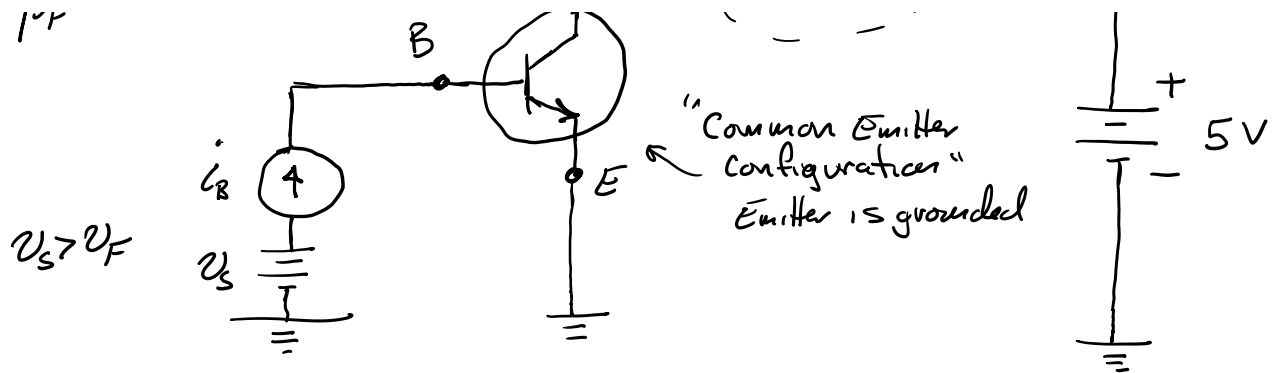

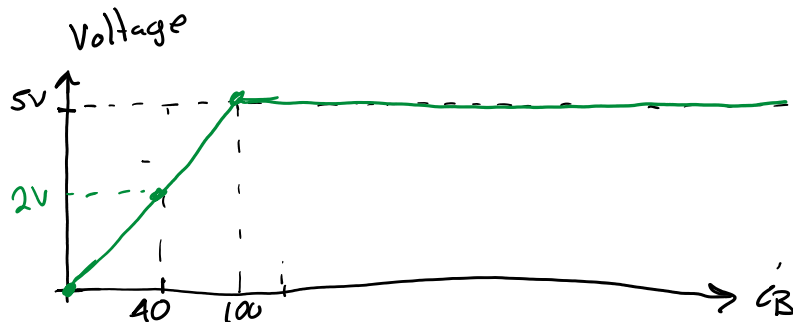Find voltage across light bulb as a function of  $i_B$ .



$$i_B = 0: i_C = \beta_F i_B \Rightarrow i_C = 0$$

$$i_B = 40 \mu A:$$

$$i_C = \beta_F i_B = 50 (40 \mu A) = 2 mA$$

$$V_C = 5V - i_C (1k\Omega) = 5V - (2mA) 1k\Omega = 3V$$

$$V_{bulb} = 5V - V_C = 5V - 3V = 2V$$

$$i_B = 100 \mu A:$$

$$i_C = \beta_F i_B = 50 (100 \mu A) = 5 mA$$

$$V_C = 5V - i_C (1k\Omega) = 5 - (5mA) 1k\Omega = 0$$

At saturation threshold

$$V_{bulb} = 5V - V_C = 5V$$


$$i_B = 200 \mu A: \text{ In deep saturation } i_B > i_{Bsat}$$

$i_C$  remains at closed switch current level

MOSFET

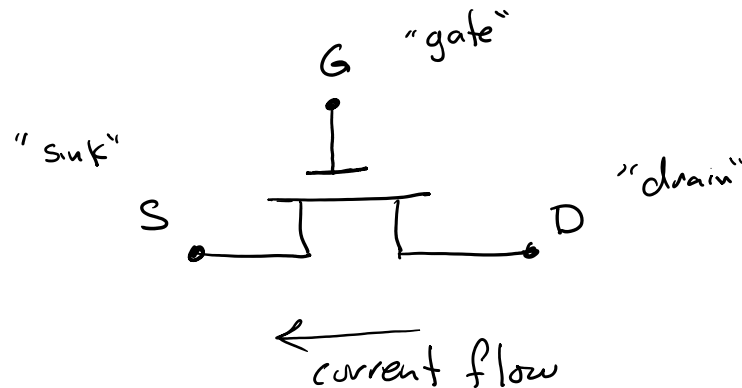
# MOSFET

Often used as variable resistors (but there are other creative uses).




No current flow through the gate.

current-voltage relationship:

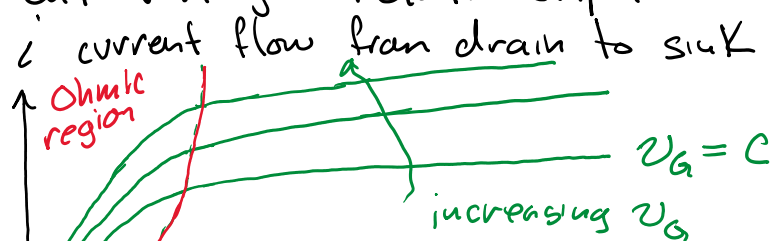

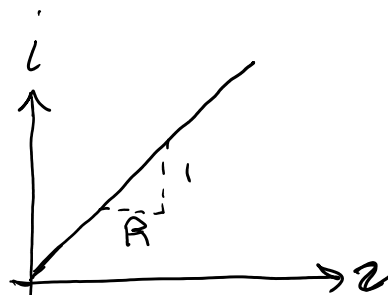MOSFET behaves like a resistor in Ohmic region.  
Effective resistance is controlled by  $V_G$ .



$$v = iR \\ \Rightarrow i = \frac{1}{R} v$$

We'll cover an example application when discussing LED driver circuits.

we'll cover an example application when discussing  
LED driver circuits.