

Electro - Optics


Will consider:

1. LEDs: Light Emitting Diodes
2. Phototransistor

LED


Used as indicator lights and illumination.

current-voltage relationship

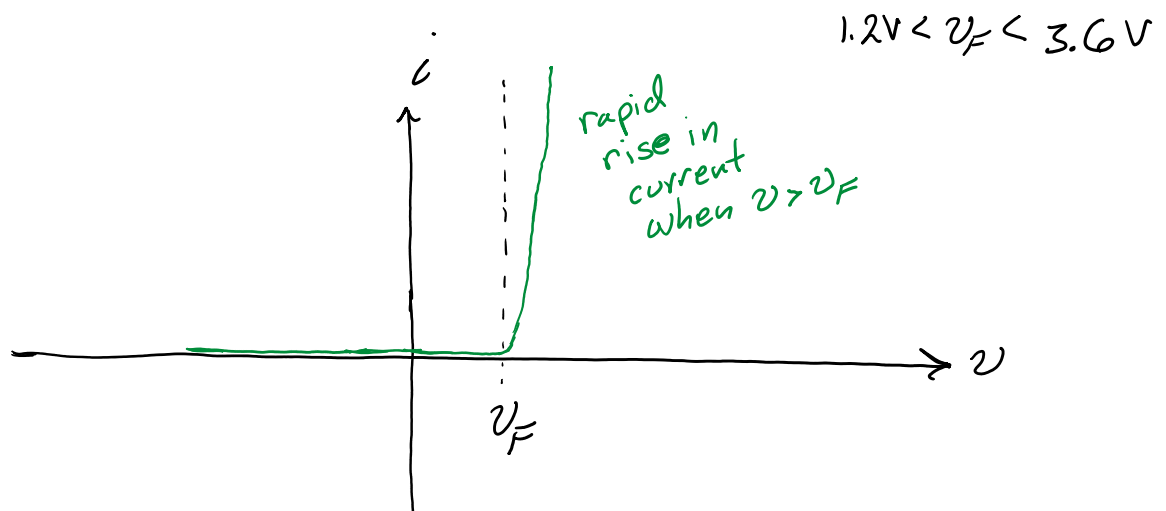

LED's act like regular diodes, but emit light and have higher activation voltages.

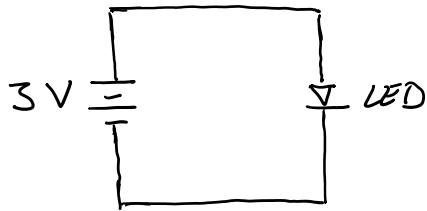
Suppose we want to use an LED. How to setup a circuit to drive the LED?



$$V_F = 2.7V$$

The problem with this is that the current flow will likely exceed the max allowable current of the LED.

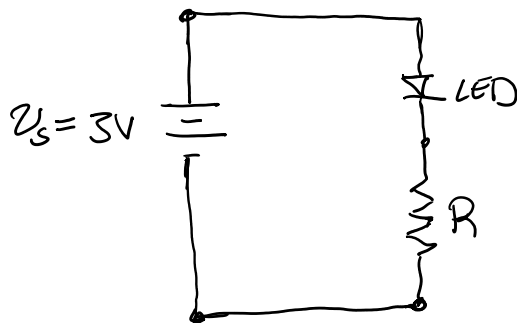An easy fix: add a resistor in series with the LED






Resistor limits current flow.

For analysis, assume voltage across LED is $\approx V_F$. Then select R such that

$$i = \frac{V_s - V_F}{R} < i_{max}$$

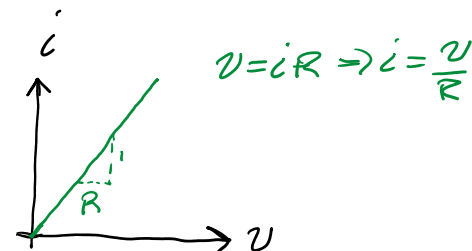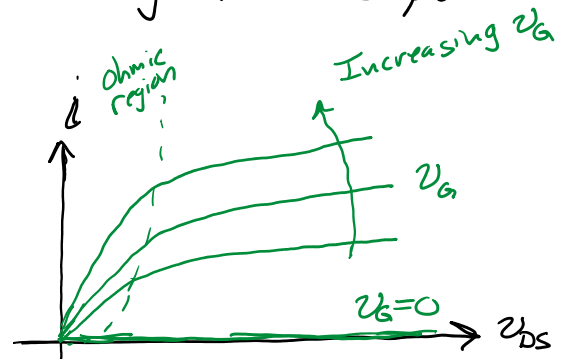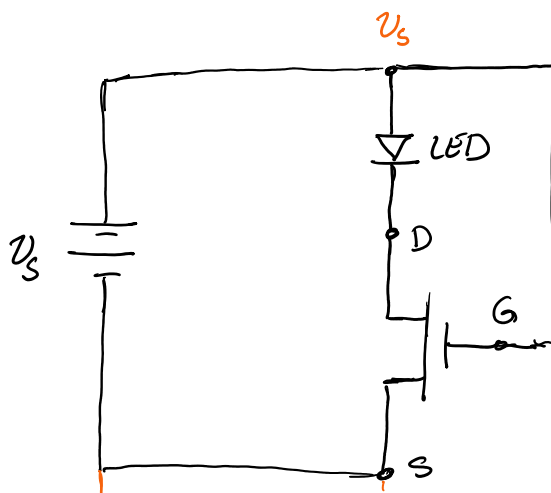This works, but it lacks efficiency. We lose power due to the resistor R.




Holds
MOSFET
at min R



MOSFET
at min R

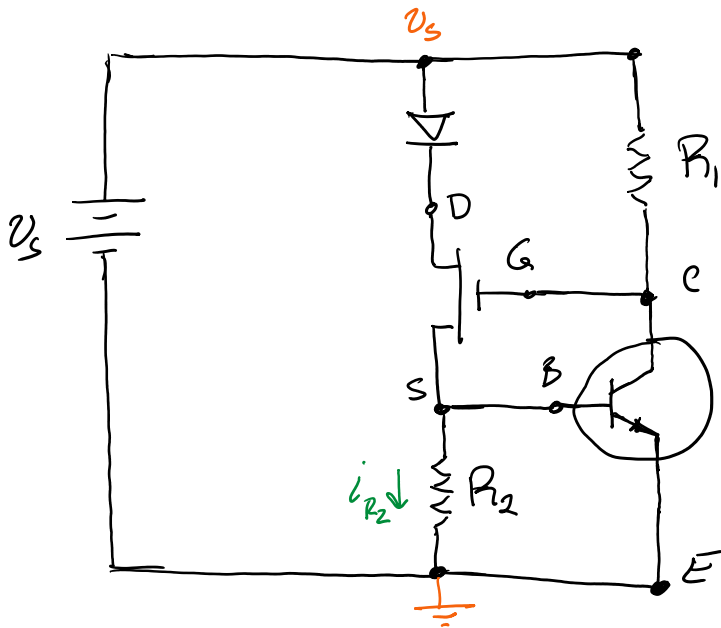Let $i_* < i_{max}$ is the max allowable current flow through the LED



Size R_2 s.t. the voltage at the top of R_2 equals the activation voltage of the NPN when $i_{R_2} = i_*$

How this works:

1. When $i_{R_2} < i_*$,

No current flow from C to E through NPN

Never current flow through gate of MOSFET

No current flow through R_1

Gate voltage is $V_G = V_s$.

$$i_{LED} = i_{R_2} < i_*$$

2. When $i_{LED} = i_*$

a) NPN goes into active state & acts as a current amp.

- a) NPN goes into active state & acts as a current amp.
- b) NPN draws current flow through R_1
- c) Gate voltage drops due to voltage drop across R_2
- d) Effective resistance of the MOSFET increases
- e) Current flow through LED is limited by increased resistance of MOSFET