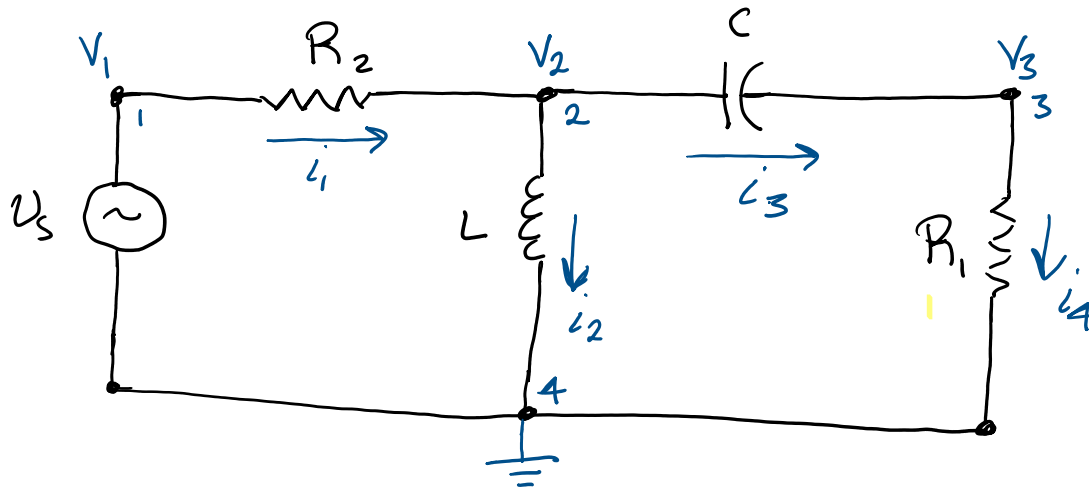


AC Circuit Analysis

Consider the 2 mesh



Start with node 2 and apply KCL,

$$I_1 - I_2 - I_3 = 0$$

$$\Rightarrow -\frac{V_2 - V_1}{R_2} - I_2 - C \frac{d}{dt} [V_2 - V_3] = 0$$

Differentiate,

$$-\frac{1}{R_2} \frac{dV_2}{dt} + \frac{1}{R_2} \frac{dV_1}{dt} - \frac{dI_2}{dt} + C \frac{d^2 V_3}{dt^2} - C \frac{d^2 V_2}{dt^2} = 0$$

$$\frac{dI_2}{dt} = \frac{1}{L} (V_1 - 0) = \frac{V_2}{L}$$

\therefore

$$-\frac{1}{R_2} \frac{dV_2}{dt} + \frac{1}{R_2} \frac{dV_1}{dt} - \frac{1}{L} V_2 + C \frac{d^2 V_3}{dt^2} - C \frac{d^2 V_2}{dt^2} = 0$$

Now,

$\therefore \dots$

Now,

$$\begin{aligned} V_1 &= V_{01} e^{j\omega t} \\ V_2 &= V_{02} e^{j(\omega t + \phi_2)} = V_{02} e^{j\phi_2} e^{j\omega t} \\ V_3 &= V_{03} e^{j(\omega t + \phi_3)} = V_{03} e^{j\phi_3} e^{j\omega t} \end{aligned}$$

Substitute & factor out $e^{j\omega t}$

$$\left[-\frac{j\omega}{R_2} V_{02} e^{j\phi_2} + \frac{j\omega}{R_2} V_{01} e^{j\phi_1} - \frac{1}{L} V_{02} e^{j\phi_2} + (-\omega^2) C V_{03} e^{j\phi_3} - (-\omega^2) C V_{02} e^{j\phi_2} \right] e^{j\omega t} = 0$$

Observation 1: When we substitute $V = V_0 e^{j\omega t} e^{j\phi}$ the $e^{j\omega t}$ will always be a common factor & divide out. The only part that matters,

$$V_0 e^{j\phi}$$

Likewise, $I = I_0 e^{j\omega t} e^{j\phi}$, we only need $I_0 e^{j\phi}$.

Given a harmonic function (harmonic signal)


$$X(t) = X_0 e^{j\phi} e^{j\omega t}$$

define the "phasor" of the function as


$$\bar{X} = X_0 e^{j\phi}$$

\nwarrow phasor \nearrow amplitude
 \nwarrow phase angle

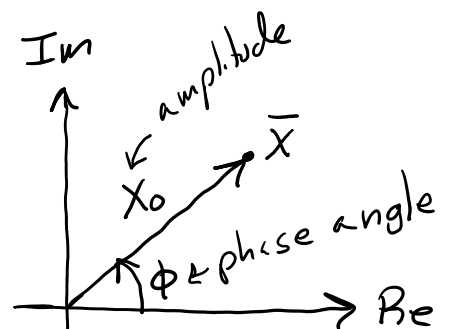A phasor is just a complex number that encodes




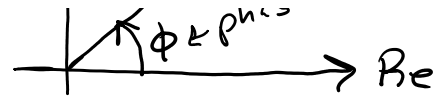amplitude
A phasor is just a complex number that encodes amplitude & phase information.



Phasor relationships for common circuit elements

Inductor

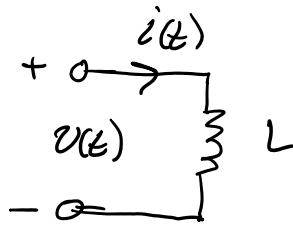

$$v(t) = L \frac{di}{dt}$$


$$\Rightarrow v(t) = L \frac{dI}{dt}$$

$$\Rightarrow V_0 e^{j\theta} e^{j\omega t} = L \frac{d}{dt} [I_0 e^{j\phi} e^{j\omega t}]$$


$$\Rightarrow V_0 e^{j\theta} = j\omega L I_0 e^{j\phi}$$

$$\Rightarrow V_0 e^{j\theta} = j\omega L I_0 e^{j\phi}$$
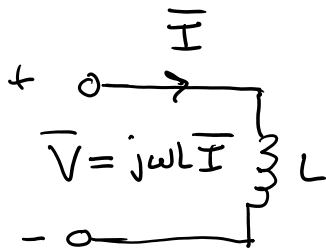
$$\Rightarrow \bar{V} = j\omega L \bar{I}$$



Capacitor:

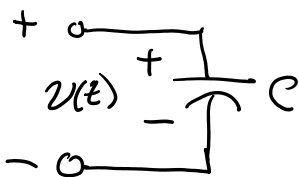


$$i(t) = C \frac{dv}{dt}$$

$$\Rightarrow I_0 e^{j\theta} e^{j\omega t} = C \frac{d}{dt} [V_0 e^{j\phi} e^{j\omega t}]$$

$$\Rightarrow I_0 e^{j\theta} = j\omega C V_0 e^{j\phi}$$


$$\Rightarrow \bar{I} = j\omega C \bar{V}$$
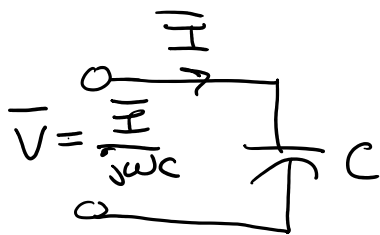
$$\Rightarrow \bar{V} = \frac{1}{j\omega C} \bar{I}$$



Resistor:


Resistor:

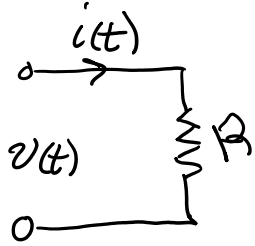

$$v(t) = i(t) R$$

$$\Rightarrow V_0 e^{j\phi} \cancel{e^{j\omega t}} = I_0 e^{j\phi} \cancel{e^{j\omega t}} R$$

$$\Rightarrow \bar{V} = \bar{I} R$$

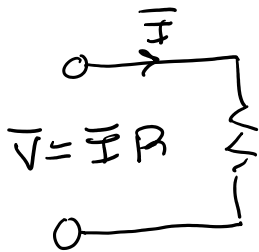

Define "impedance" of a circuit element as

$$\bar{Z} = \frac{\bar{V}}{\bar{I}}$$

\uparrow impedance \nwarrow voltage phasor \swarrow current phasor

Impedance is a resistance-like quantity and it has units of Ohms.

Impedance of common circuit elements

Capacitor:

$$\bar{V} = \frac{1}{j\omega C} \bar{I} \Rightarrow \bar{Z}_C = \frac{\bar{V}}{\bar{I}} = \frac{1}{j\omega C}$$

Inductor

$$\bar{V} = j\omega L \bar{I} \Rightarrow \bar{Z}_L = \frac{\bar{V}}{\bar{I}} = j\omega L$$


Resistor

$$\bar{Z}_R = \frac{\bar{V}}{\bar{I}} = R$$

Resistor

$$\bar{V} = \bar{I} R \quad \Rightarrow \quad \bar{Z}_R = \frac{\bar{V}}{\bar{I}} = R$$

Return to the original circuit

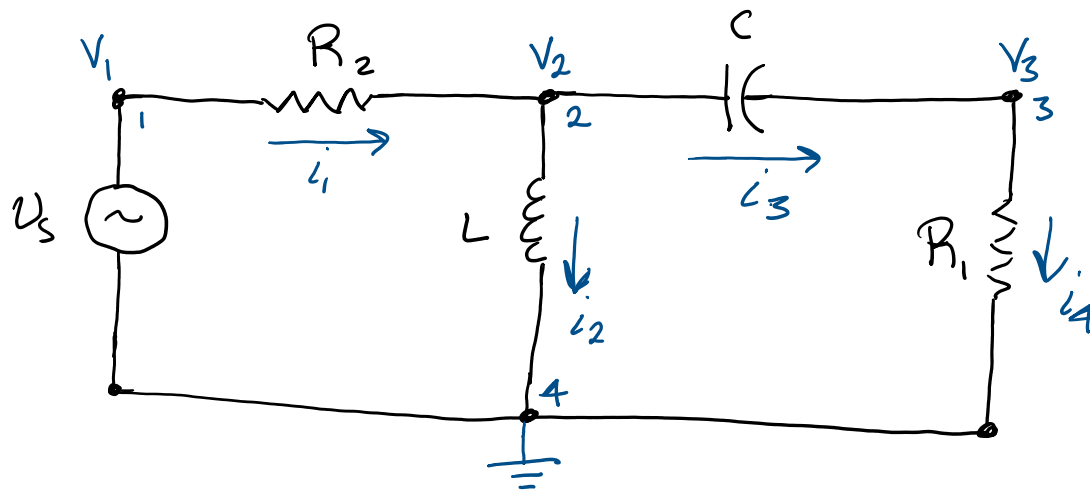

Node 2:

$$\bar{I}_1 - \bar{I}_2 - \bar{I}_3 = 0$$

$$\Rightarrow \frac{\bar{V}_1 - \bar{V}_2}{\bar{Z}_{R_2}} - \left[\frac{\bar{V}_2 - 0}{\bar{Z}_L} \right] - \left[\frac{\bar{V}_2 - \bar{V}_3}{\bar{Z}_C} \right] = 0$$

$$\Rightarrow \frac{\bar{V}_1 - \bar{V}_2}{R_2} - \frac{\bar{V}_2}{j\omega L} - \frac{\bar{V}_2 - \bar{V}_3}{\frac{1}{j\omega C}} = 0$$

$$\Rightarrow \left(\frac{1}{j\omega L} + j\omega C + \frac{1}{R_2} \right) \bar{V}_2 - j\omega C \bar{V}_3 = \frac{1}{R_2} \bar{V}_1$$

Node 3:

$$\bar{I}_3 - \bar{I}_4 = 0$$

$$\Rightarrow \frac{\bar{V}_2 - \bar{V}_3}{\bar{Z}_C} - \frac{\bar{V}_3}{R_1} = 0$$

$$\Rightarrow \frac{\overline{V_2 - V_3}}{\frac{1}{j\omega C}} - \frac{\overline{V_3}}{R_1} = 0$$

$$\Rightarrow j\omega C \overline{V_2} - (j\omega C + R_1) \overline{V_3} = 0$$

2 equations, 2 unknowns

Solve for $\overline{V_2}$ and $\overline{V_3}$