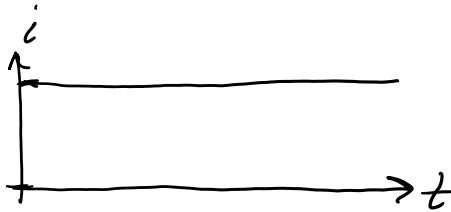



# AC Circuits

DC:




No change in current flow direction

AC:

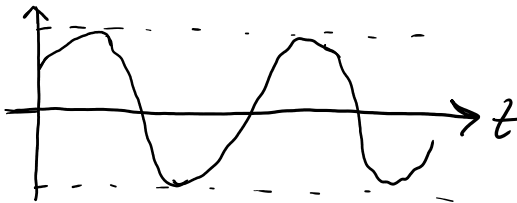

current flow oscillates (changes direction)

Why AC?

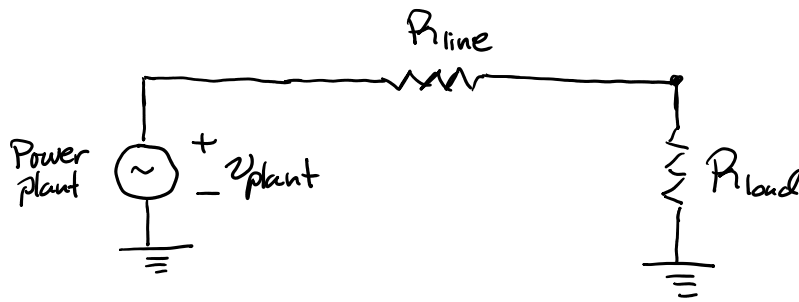

$$P_{loss} = i^2 R_{line}$$

$$P_{in} = i v_{plant}$$


$\therefore$

$$P_{loss} = \left( \frac{P_{in}}{v_{plant}} \right)^2 R_{line}$$

$$P_{loss} \rightarrow 0 \quad \text{when} \quad v_{plant} \rightarrow \infty$$

Faraday's Law: "The induced voltage in a coil is proportional to the rate of change of magnetic flux through the coil"

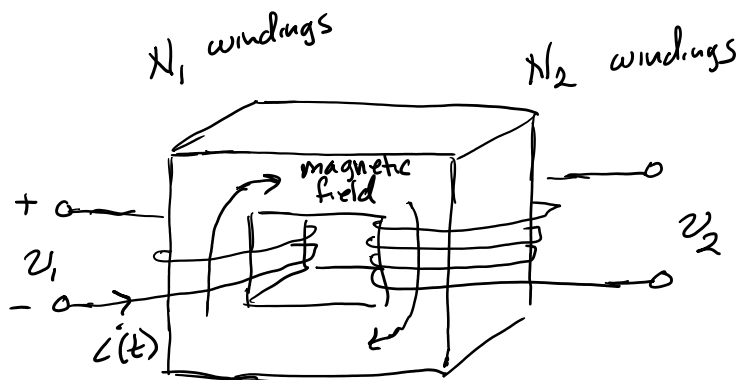
Faraday's Law: "The induced voltage in a coil is proportional to the time rate of change of flux linkage."



$$\frac{v_2}{v_1} = \frac{N_1}{N_2}$$

But this only works  
if  $i$  is time varying  
 $\frac{di}{dt} \neq 0$

Consider again an RLC circuit,

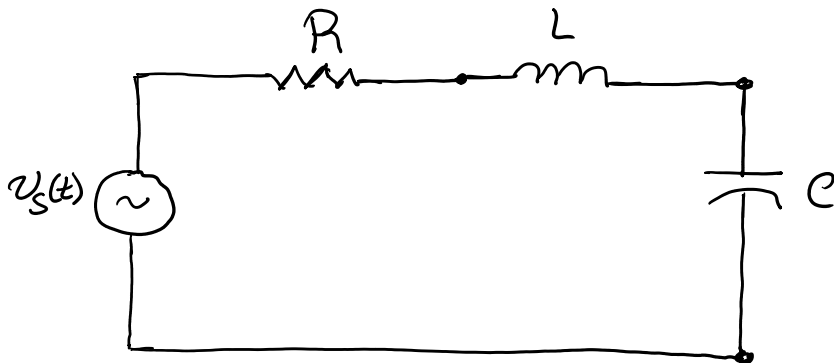

What is the current flow  $i(t)$  if  $v_s(t) = V_0 \sin(\omega t)$

From last lecture,

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{dv_s}{dt} = \underbrace{\omega V_0 \cos(\omega t)}_{F_0}$$

$$= \underbrace{F_0}_{F_0} \cos(\omega t)$$

Recall from ODE's

The solution is

$$i(t) = i_H(t) + i_p(t)$$

$\uparrow$  Homogeneous solution       $\uparrow$  particular solution

If we want to know the "steady-state" response ( $t \rightarrow \infty$ ), we know

$$i_H(t) \rightarrow 0 \quad \text{as } t \rightarrow \infty \quad R > 0$$

So, the steady-state solution

$$i(t) = i_p(t)$$

For harmonic forcing,

$$i_p(t) = I_0 \cos(\omega t + \phi)$$

Observe,

$$\begin{aligned}
 F(t) &:= F_0 \cos(\omega t) + j F_0 \sin(\omega t) \\
 &= F_0 e^{j\omega t} \quad ; \quad e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)
 \end{aligned}$$

Now,

$$I(t) = i(t) + j \varphi(t)$$

Then

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = F$$

$$\Rightarrow \left[ \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i \right] + j \left[ \frac{d^2 \varphi}{dt^2} + \frac{R}{L} \frac{d\varphi}{dt} + \frac{1}{LC} \varphi \right]$$

$$= F_0 \cos \omega t + j F_0 \sin \omega t$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = F_0 \cos \omega t \quad !$$

i.e.

We can represent any physical harmonic forcing by a complex function of the form

$$A e^{j\omega t}$$

and the real component of the solution will correspond to the physical response.

Since the forcing has the form  $F_0 e^{j\omega t}$ ,

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = F_0 e^{j\omega t}$$

Know, the steady sol'n

$$I(t) = I_0 e^{j(\omega t + \phi)}$$

Note:  
 $j = \sqrt{-1}$   
 $j^2 = -1$


Substitute  $I$  into ODE,

$$-\omega^2 I_0 e^{j(\omega t + \phi)} + \frac{R}{L} j\omega I_0 e^{j(\omega t + \phi)} + \frac{1}{LC} I_0 e^{j(\omega t + \phi)} = F_0 e^{j\omega t}$$

$$\Rightarrow [-\omega^2 + j\omega \frac{R}{L} + \frac{1}{Lc}] I_0 e^{j\omega t} e^{j\phi} = F_0 e^{j\omega t}$$

$$\Rightarrow I_0 e^{j\phi} = \frac{F_0}{(\frac{1}{Lc} - \omega^2) + j(\omega \frac{R}{L})}$$

Recall:

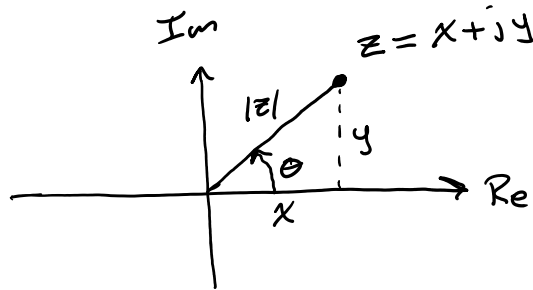

$$z = |z| e^{j\theta} = x + jy$$

$$|z|^2 = x^2 + y^2$$

$$\tan \theta = \frac{y}{x}$$

$\therefore$

$$\begin{aligned} I_0 e^{j\phi} &= \frac{F_0}{\sqrt{(\frac{1}{Lc} - \omega^2)^2 + (\omega \frac{R}{L})^2}} \\ &= \frac{F_0}{\sqrt{(\frac{1}{Lc} - \omega^2)^2 + (\omega \frac{R}{L})^2}} e^{-j\theta} \end{aligned}$$

$\therefore$

$$I_0 = \frac{F_0}{\sqrt{(\frac{1}{Lc} - \omega^2)^2 + (\omega \frac{R}{L})^2}}$$

$$\phi = \tan^{-1} \left( - \frac{\omega \frac{R}{L}}{\frac{1}{Lc} - \omega^2} \right)$$